

167181 - PART A

Calculations in series

- a) Total resistance in ohms
 $= 20 + 30 + 50 = 100\text{ohms}$
- b) Total Current from the power supply
 $V = IR$
 $125 = I100$
 $I = 125/100$
 $I = 1.25\text{A}$
- c) Calculate the current through each resistor
In a series circuit, current is the same through all the resistors hence 1.25A
- d) Calculate the voltage drop in each resistor
In 20ohms, ($V=IR$) $20 \times 1.25 = 25\text{V}$
In 30ohms, ($V=IR$) $30 \times 1.25 = 37.5\text{V}$
In 50ohms, ($V=IR$) $50 \times 1.25 = 62.5$
- e) Calculate the power dissipated through each resistor ($\text{Power} = VI$)
In 20ohms, ($P=VI$) $25 \times 1.25 = 31.25\text{w}$
In 30ohms, ($P=VI$) $37.5 \times 1.25 = 46.875\text{w}$
In 50ohms, ($P=VI$) $62.5 \times 1.25 = 78.125\text{w}$

Calculations in parallel

- f) Total resistance in ohms
 $= 1/\text{Total Resistance} = 1/20 + 1/100 + 1/50 = 0.08$
 $1/\text{Total resistance} = 8/100$
 $\text{Total resistance} = 100/8 = 12.5$
 $= 12.5 \text{ ohms}$
- g) Total Current from the power supply
 $V = IR$
 $125 = I12.5$
 $I = 125/12.5$
 $I = 10\text{A}$
- h) Calculate the current through each resistor
In a parallel circuit, voltage is the same through all the resistors hence 125V
 $V=IR$
In 20ohms, ($125=20I$) $125/20=6.25\text{A}$
In 100ohms, ($125=100I$) $125/100=1.25\text{A}$
In 50ohms, ($125=50I$) $125/50=2.5\text{A}$
- i) Calculate the voltage drop in each resistor
In a parallel circuit, Voltage is the same in each resistor
hence= 125V

j) Calculate the power dissipated through each resistor (Power =VI)

In 20ohms, (P=VI) $125 \times 6.25 = 781.25\text{w}$

In 100ohms, (P=VI) $125 \times 1.25 = 156.25\text{w}$

In 50ohms, (P=VI) $125 \times 2.5 = 312.5\text{w}$

Part B

Component Table list in Series

Component Reference Name	Component	Value	Quantity
V	DC Voltage source	125v	1
R1	Resistor	20	1
R2	Resistor	30	1
R3	Resistor	50	1
-	Connecting wires	-	4
-	Ground	-	1

Component Table list in Parallel

Component Reference Name	Component	Value	Quantity
V	DC Voltage source	125v	1
R4	Resistor	20	1
R5	Resistor	100	1
R6	Resistor	50	1
-	Connecting wires	-	6
-	Ground	-	1

Component table for DHT22 and Arduino

Component Reference Name	<u>Component</u>	<u>Value</u>	<u>Quantity</u>
<u>Arduino Nano V3</u>	<u>Microcontroller</u>	=	<u>1</u>
<u>DHT22</u>	<u>Temperature and Humidity sensor</u>	=	<u>1</u>
	<u>Connecting wires</u>	=	<u>4</u>